

Quantization theory

- ① Quantization: transformation of analog signals to discrete outputs
- ② Coding: Assign the outputs to a digital code.

Analog - to - Digital converters (A/D)

8-bit, 10-bit, 12-bit, ...

Resolution : 2^n n : bits of A/D converter.

Example 1: 3-bit A/D : $2^3 = 8$ levels. (Resolution)

Example 2:

The input voltage is in the range of 0 - 4 V. How can we use a 3-bit A/D converter to analyze the input voltage

Number of levels = $2^3 = 8$

Quantization

Coding


Voltage	State	Binary code
0-0.5	1	000
0.5-1	2	001
1-1.5	3	010
1.5-2	4	011
2-2.5	5	100
2.5-3	6	101
3-3.5	7	110
3.5-4	8	111

- Input voltage = 3.2 V \Rightarrow Code 110

- Quantization size = $\frac{V_{max} - V_{min}}{2^n} \Rightarrow \frac{4 - 0}{2^3} = 0.5V$


Using a 10-bit $\Rightarrow \frac{4 - 0}{2^{10}} \approx 0.0004 V$

Analog - to - Digital Conversion

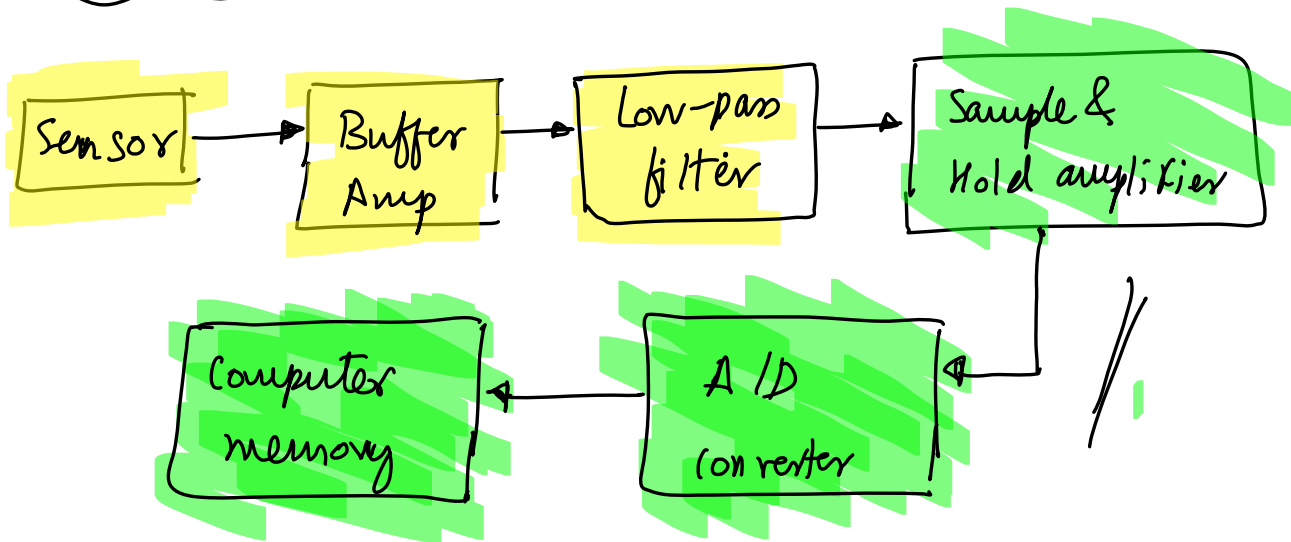

1) Sensor: measures physical quantity & converts to voltage

2) Buffer amp:

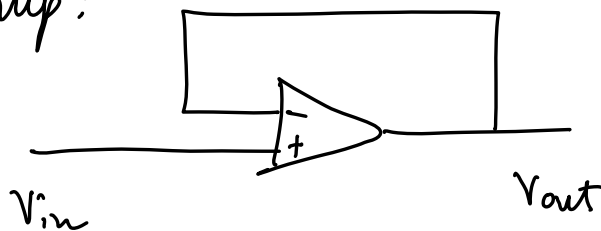


a) non-inverting op-amp

b) amplify & isolate the output from input

3) low-pass filter: assumes the V_{in} has high frequency noise

(RC)

4) Sample and hold amplifier

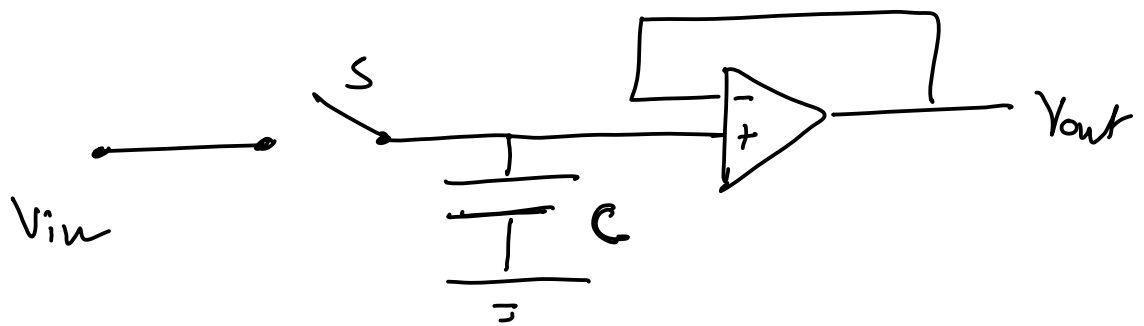

holds the input for the A/D & compute memory

5) A/D converter

- convert analog signal to digital signal


6) Computer memory

save data.

Analog to Digital Converters

- ① Successive approximation converter
- ② Flash Converter

① Successive approximation converter

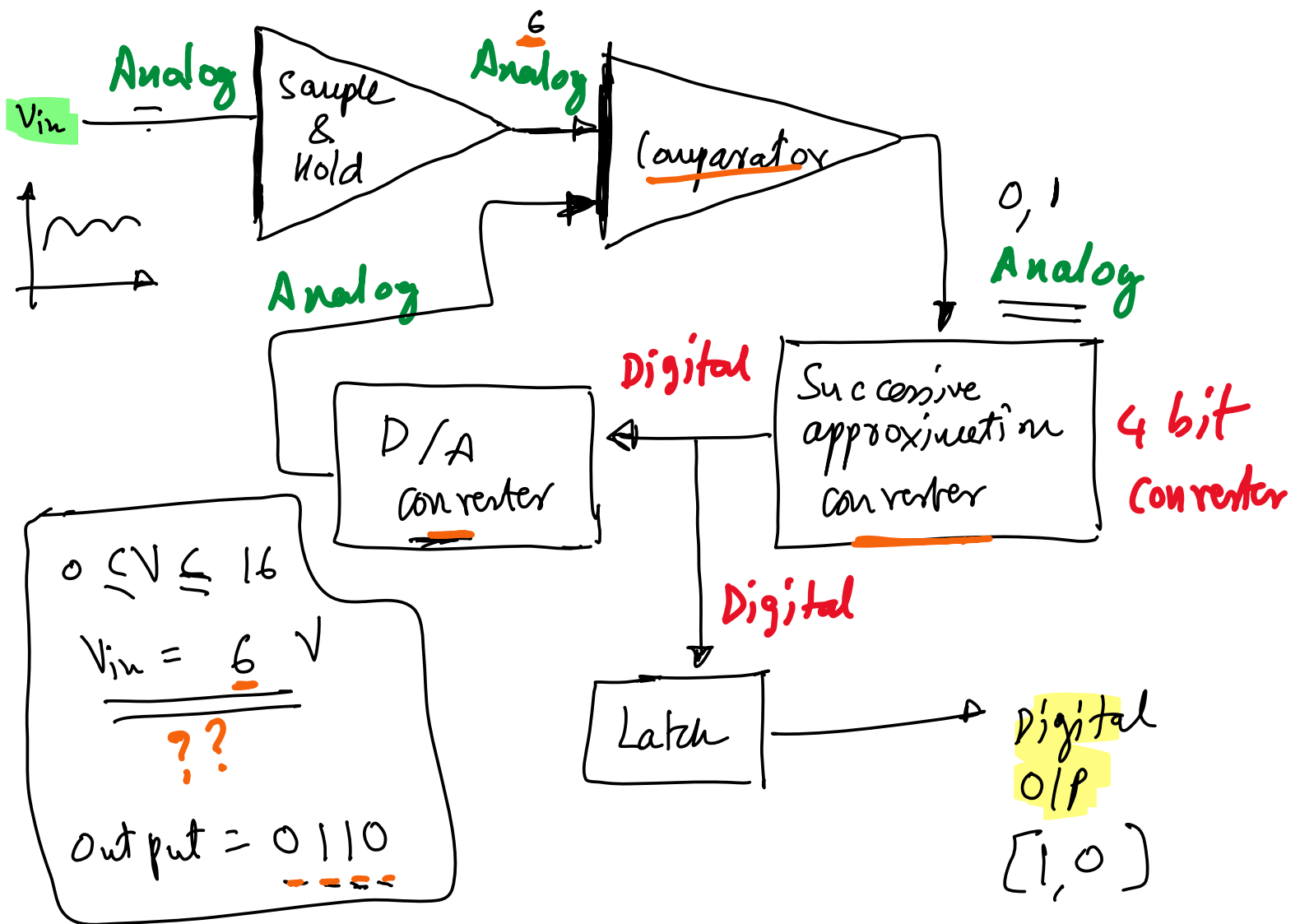



Hand-drawn marks resembling a stylized signature or symbol.

$$\checkmark$$

$$6V \Rightarrow \overset{3}{0} \overset{2}{1} \overset{1}{1} \overset{0}{0}$$

$$\underline{\underline{0(2^3) + 1(2^2) + 1(2^1) + 0(2^0)}} = 0 + 4 + 2 + 0 = 6 \quad \checkmark$$

Working

① $V_{in} = 6V$
 comparator: compare $6V$ against $\frac{1}{2^1}(16)$ $0-16V$
↓

$$6V < 8V$$

output = 0

② comparator: compare $6V$ against $\frac{1}{2^2}(16)$

$$6V \geq \underline{4V}$$

output = 1

③ comparator: compares $6V$ against $\frac{1}{2^3}(16+4)$

$$6V \geq \underline{6V} \quad \text{D/A}$$

output = 1

④ compare $6V$ against $6 + \frac{1}{2^4} (16) =$

$$6V \leq 7V$$

$$\text{output} = \underline{\underline{0}}$$

From ①, ②, ③, ④

Digital output = 0 1 1 0



⇒ It took 4 cycles to interpret the 4 digits. For n -bits, it will take a time of nT

↻ clock

This is time consuming (DIS)

⇒ ADVANTAGE: Require very few electronic components.